



## **FACULTY OF COMPUTING AND INFORMATICS**

### **DMA5301 DISCRETE STRUCTURES TRIMESTER 1 SESSION 2021/2022**

#### **ASSIGNMENT PART 2**

##### **GROUP:**

	<b>Name</b>	<b>Student ID</b>
<b>Leader</b>	Ayat Abdulaziz Gaber Al-Khulaqi	1191202335
<b>Members</b>	Raisa Raad Khan	1191202087
	Ove Ataul Haque	1191202480
	Sheikh Mohammed Zain	1191202496

## CHAPTER 8 & 9

A. Create your own LOGIC GATE CIRCUIT that fulfil all requirement below:

I. Must have 3 or 4 INPUT variables.

II. Circuit must have a combination of 6 to 7 logic gates with at least 3 different gates.

III. Draw the circuit and indicate the FINAL OUTPUT.

IV. Next, construct a truth table of Boolean Algebra based on your final output.

### ANSWER

i) 4 inputs - A,B,C,D

ii) 3 different Gates - NOT gate, AND gate, OR gate


Combination of 7 logic gates -

2 NOT gates

4 AND gates

1 OR gate

iii) Logic Gate Circuit:

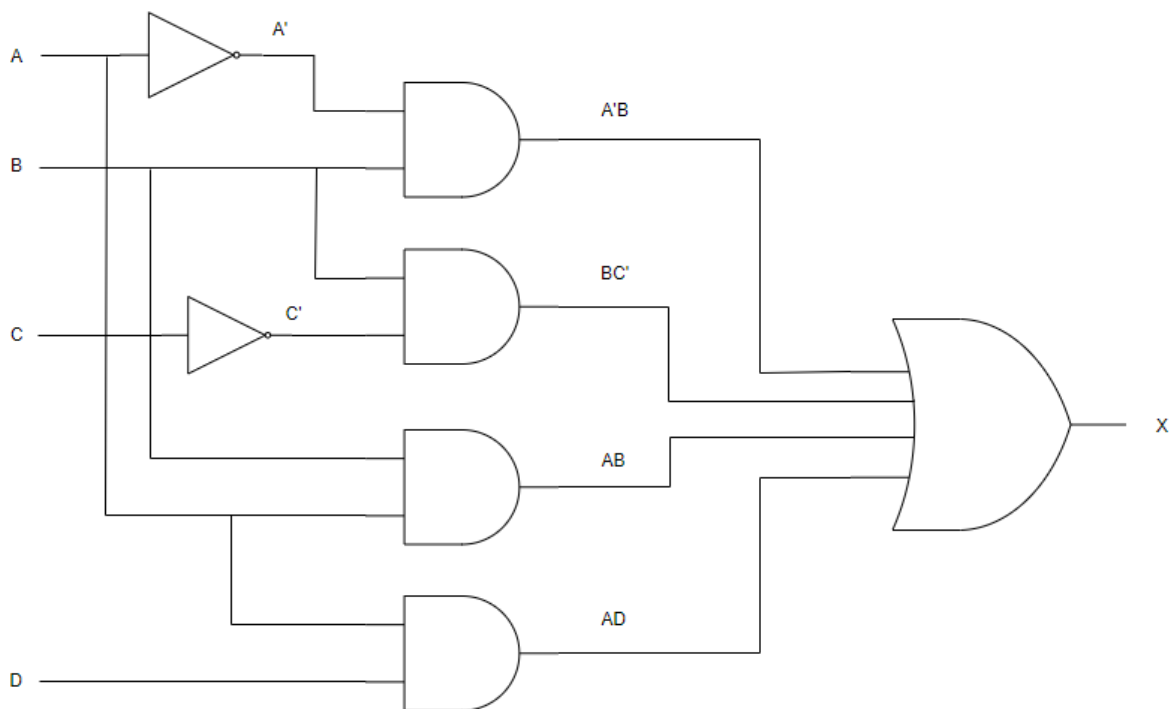

$$\text{FINAL OUTPUT: } X = (A'B) + (BC') + (AB) + (AD)$$

iv) Boolean Algebra =  $(A'B) + (BC') + (AB) + (AD)$

A	B	C	D	A'	C'	(A'B)	(BC')	(AB)	(AD)	X
0	0	0	0	1	1	0	0	0	0	0
0	0	0	1	1	1	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	0	1	1	1	0	0	0	0	0	0
0	1	0	0	1	1	1	1	0	0	1
0	1	0	1	1	1	1	1	0	0	1
0	1	1	0	1	0	1	0	0	0	1
0	1	1	1	1	0	1	0	0	0	1
1	0	0	0	0	1	0	0	0	0	0
1	0	0	1	0	1	0	0	0	1	1
1	0	1	0	0	0	0	0	0	0	0
1	0	1	1	0	0	0	0	0	1	1
1	1	0	0	0	1	0	1	1	0	1
1	1	0	1	0	1	0	1	1	1	1
1	1	1	0	0	0	0	0	1	0	1
1	1	1	1	0	0	0	0	1	1	1

B. Create your own Finite State Machine M (FSM) that satisfy all requirement below:

I. 3 inputs,  $I = \{a, b, c\}$

II. 5 states,  $S = \{S0, S1, S2, S3, S4\}$

III. Output,  $O = \{0, 1\}$

IV. Initial state S0.

a) Draw the state diagram of the machine M.

b) Construct the state table of the machine M.


c) Create one example of input string from machine M that has at least 8 strings and find the output string.

d) Can you redraw your Finite State Machine M (FSM) as a Finite State Automaton?

Why (justify your answer)?

## ANSWER

a) State Diagram:

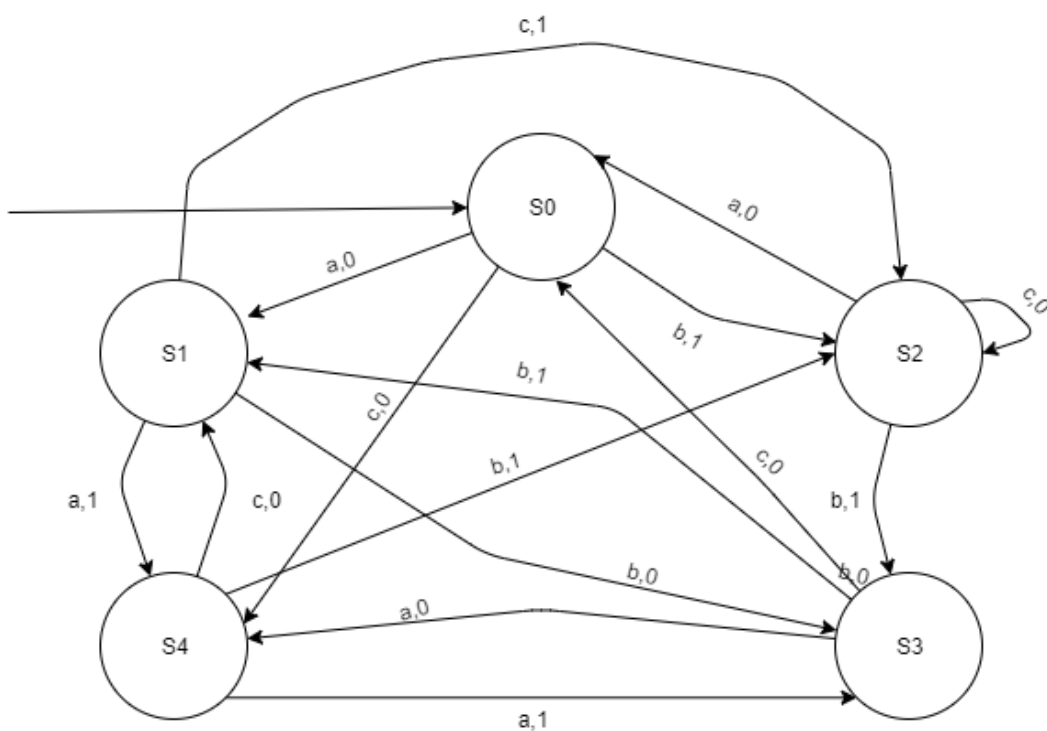

b) State Table:

	INPUTS			OUTPUTS		
State	a	b	c	a	b	c
S0	S1	S2	S4	0	1	0
S1	S4	S3	S2	1	0	1
S2	S0	S3	S2	0	1	0
S3	S4	S1	S0	0	1	0
S4	S3	S2	S1	1	1	0

c) Input String: abcbacbb

OUTPUT: 00010011

d) Can you redraw your Finite State Machine M (FSM) as a Finite State Automaton?

Answer:

The Final State Machine can not be redrawn as a Finite State Automaton as long as the outputs from all of the states are not the same individually i.e s0 is required to output 0 in all of its outputs and i.e s1 is required to output 1 on all given outputs from s1.